

CHAPTER 16
(ALTERNATING CURRENT)

1. Encircle the correct answers.

- i. If V_{rms} be the root mean square value of emf then its peak to peak value is given by:
- $\frac{V_{rms}}{\sqrt{2}}$
 - $\sqrt{2}V_{rms}$
 - $\frac{2}{\sqrt{2}V_{rms}}$
 - $\frac{V_{rms}}{2}$
- ii. The value of capacitive reactance is given by:
- $X_c = VI$
 - $X_c = \frac{V}{I}$
 - $X_c = \frac{I}{V}$
 - All of above
- iii. In case of capacitor, the unit of reactance is:
- Farad
 - Ohm
 - Newton
 - All of these
- iv. The unit of impedance is:
- Farad
 - Henry
 - Tesla
 - Ohm
- v. The natural frequency of L.C circuit is equal to:
- $\frac{1}{2\pi} \sqrt{\frac{C}{L}}$
 - $\frac{1}{2\pi} \sqrt{\frac{L}{C}}$
 - $\frac{1}{2\pi\sqrt{LC}}$
 - $\frac{\sqrt{LC}}{2\pi}$
- vi. The reactance of inductor depends upon:
- L
 - ωL
 - ω
 - All of the above
- vii. The effective value of any sinusoidal alternating current or voltage is:
- $\sqrt{3}$ times its maximum value
 - $\frac{1}{\sqrt{2}}$ time its maximum value
 - $\sqrt{2}$ times its maximum value
 - None of the above
- viii. At high frequency, the current through a capacitor is:
- Small
 - Infinity
 - Zero
 - Large
- ix. Radio frequency choke is:
- Iron cored
 - Air cored
 - Air as well as iron cored
 - None of these
- x. In frequency modulation, the amplitude of carrier waves is:
- Increases
 - Remains constant
 - Decreases
 - None of these

Q.2 Write the short answers.

- A sinusoidal current has rms(effective) value of 10 A. What is the maximum or peak value?
- Name the device that will (a) permit flow of direct current but oppose the flow of alternating current (b) permit flow of alternating current but not the direct current.
- How many times per second will an incandescent lamp reach maximum brilliance when connected to a 50 Hz source?
- A circuit contains an iron-cored inductor, a switch and a D.C. source arranged in series. The switch is closed and after an interval reopened. Explain why a spark umps across the switch contacts?
- How does doubling the frequency affect the reactance of (a) an inductor (b) a capacitor?
- Explain the conditions under which electromagnetic waves are produced from a source?
- How the reception of a particular radio station is selected on our radio set?
- Define choke and give its uses.

Note: Long questions:

Q.3 (a) What is series resonance circuit? Describe its properties. Also find the resonance frequency for the circuit.

(b) An alternating current is represented by the equation $I = 20 \sin 100 \pi t$. Compute its frequency and the maximum and rms values of current.

Q.4 (a) Explain R-c series circuit. Find its impedance and also fine its phase.

(b) What is the resonant frequency of a circuit which includes a coil of inductance 2.5 H and a capacitance $40 \mu\text{F}$?