

## CHAPTER 18 ELECTRONICS

### 1. Encircle the correct answers.

- i. The average gap for Germanium at 0K is:
- 1.12 eV
  - 0.02 eV
  - 6.72 eV
  - 7.2 eV
- ii. The impurity in the germanium is usually in the ratio of:
- $1:10^6$
  - $1:10^4$
  - $1:10^8$
  - $1:10^{10}$
- iii. In a certain circuit,  $I_B = 40 \mu\text{A}$ ,  $I_C = 20 \text{ mA}$ :
- 450 amp
  - 0.45 amp
  - 5 mA
  - 500 amp
- iv. For normal transistor the emitter current can be given by:
- $I_E = I_C$
  - $I_E = I_C + I_B$
  - $I_E = I_B$
  - None of these
- v. In case of op-amp as an inverting amplifier,  $V_+ - V_- = 0$ , this is because:
- Open gain loop is very low
  - Closed loop gain is very high
  - Open loop gain is very high
  - Both (a) and (b)
- vi. An expression for gain of an inverting amplifier is:
- $-\frac{R_2}{R_1}$
  - $\frac{R_1}{R_2}$
  - $(R_1 R_2)$
  - None of these
- vii. The mathematical symbol for NOR operation is:
- $X = A + B$
  - $X = A.B$
  - $X = A + D$
  - $X = \overline{A.B}$
- viii. The gate, which changes the logic level to its opposite level is called:
- NOR gate
  - AND gate
  - OR gate
  - NOT gate
- ix. One use of a single p-n junction semiconductor in an electrical circuit is
- Rectifier

- Transistor
  - Battery
  - Diode
- x. The output from a full wave rectifier is:
- An ac voltage
  - A dc voltage
  - Zero
  - A pulsating unidirectional voltage

### Q.2 Write the short answers.

- How does the motion of an electron in n-type substance differ from the motion of holes in a p-type substance?
- What is the net charge on a n-type or a p-type substance?
- The anode of a diode is 0.2 V positive with respect to its cathode. Is it forward-biased?
- Why charge carriers are not present in the depletion region?
- Why ordinary silicon diodes do not emit light?
- Why a photo diode is operated in reverse biased state?
- What is the principle of virtual ground? Apply it to find the gain of an inverting amplifier.
- What is potential barrier? What is the value of potential barrier for Si and Ge?

### Note: Long questions:

**Q.3 (a)** How n-p-n transistor works as an amplifier. Giving its circuit diagram deduce the relation for current gain and voltage gain.

**(b)** The current flowing into the base of a transistor is  $100 \mu\text{A}$ . Find its collector current  $I_C$ , its emitter current  $I_E$  and the ratio  $I_C/I_E$ , if the value of current gain  $\beta$  is 100.

**Q.4 (a)** What is meant by rectification? Explain the action of a semi-conductor diode as half wave rectifier.

**(b)** Figure shows a transistor which operates a relay as the switch S is closed. The relay is energized by a current of 10 mA. Calculate the value  $R_B$  which will just make the relay operate. The current gain  $\beta$  of the transistor is 200. When the transistor conducts, its  $V_{BE}$  can be assumed to be 0.6V.