

# AAFAQ ACADEMY KASUR

Physics Book II

Chapter (18) NEW  
ELECTRONICS

Objective + Subjective

Test Session 2014 – Name : \_\_\_\_\_ Roll No: (in words) \_\_\_\_\_

## OBJECTIVE

Time: 10 Minutes

Marks: 10

Note: Write your roll No. in space provided.  
Over-writing, cutting, erasing, using of lead pencils will result into loss of marks.

Q.1: Encircle the correct answers.

- i. The average gap for Germanium at 0K is:  
a) 1.12 eV  
b) 0.02 eV  
c) 6.72 eV  
d) 7.2 eV
- ii. The impurity in the germanium is usually in the ratio of:  
a)  $1:10^6$   
b)  $1:10^4$   
c)  $1:10^8$   
d)  $1:10^{10}$
- iii. In a certain circuit,  $I_B = 40 \mu A$ ,  $I_C = 20 \text{ mA}$ , then the emitter current will be  
a) 450 A  
b) 0.45 A  
c) 5 mA  
d) 500 A
- iv. For normal biasing of transistor, the emitter current can be given by:  
a)  $I_E = I_C$   
b)  $I_E = I_C + I_B$   
c)  $I_E = I_B$   
d) None of these
- v. In case of op-amp as an inverting amplifier,  $V_+ - V_- = 0$ , this is because:  
a) Open loop gain is very low  
b) Closed loop gain is very high  
c) Open loop gain is very high  
d) Both (a) and (b)
- vi. An expression for gain of an inverting amplifier is:  
a)  $-\frac{R_2}{R_1}$   
b)  $\frac{R_1}{R_2}$   
c)  $(R_1 R_2)$   
d) None of these
- vii. The mathematical symbol for NOR operation is:  
a)  $X = A + B$   
b)  $X = A.B$   
c)  $X = \overline{A + B}$   
d)  $X = \overline{A.B}$

- viii. The gate, which changes the logic level to its opposite level is called:  
a) NOR gate  
b) AND gate  
c) OR gate  
d) NOT gate
- ix. One use of a single p-n junction semiconductor in an electrical circuit is a:  
a) Rectifier  
b) Transistor  
c) Battery  
d) Diode
- x. The output from a full wave rectifier is:  
a) An ac voltage  
b) A dc voltage  
c) Zero  
d) A pulsating unidirectional voltage

## SUBJECTIVE

Time: 30 min.

Marks: 20

Q.2: Write the short answers. (2 × 6)

- i. How does the motion of an electron in n-type substance differ from the motion of holes in a p-type substance?
- ii. What is the net charge on a n-type or a p-type substance?
- iii. The anode of a diode is 0.2 V positive with respect to its cathode. Is it forward-biased?
- iv. Why charge carriers are not present in the depletion region?
- v. Why ordinary silicon diodes do not emit light?
- vi. Why a photo diode is operated in reverse biased state?
- vii. What is the principle of virtual ground? Apply it to find the gain of an inverting amplifier.
- viii. What is potential barrier? What is the value of potential barrier for Si and Ge?

Note: Long questions:

Q.3 (a) How n-p-n transistor works as an amplifier? Giving its circuit diagram deduce the relation for current gain and voltage gain. (5)

(b) The current flowing into the base of a transistor is  $100 \mu A$ . Find its collector current  $I_C$ , its emitter current  $I_E$  and the ratio  $I_C/I_E$ , if the value of current gain  $\beta$  is 100. (3)