

**CHAPTER NO. 13**  
**CURRENT ELECTRICITY**

**1. Encircle the correct answers.**

- i. When a pot difference of 4 volt is applied across resistance, 10 J of energy is converted. Find charge flows.
- 0.2. C
  - 2.5 C
  - 5.0 C
  - 10.0 C
- ii. If a charge Q flows through any cross section of the conductor in time t, the current I is:
- $I = Qt$
  - $I = \frac{Q}{t}$
  - $I = \frac{t}{Q}$
  - $I = \frac{Q^2}{t}$
- iii. During electrolysis process, density of  $\text{CuSO}_4$  solution.
- Remains constant
  - Decreased
  - Increased
  - None of these
- iv. For non-ohmic devices, the graph between V and I is:
- Not a straight line
  - A straight line
  - A curve
  - All of above
- v. If there is no fourth band, tolerance is shoes as:
- $\pm 10\%$
  - $\pm 20\%$
  - $\pm 5\%$
  - 10%
- vi. The resistivity of \_\_\_\_\_ decrease with the increase in temp.
- Gold
  - Silver
  - Copper
  - Silicon
- vii. A rheostat can be used as variable resistor as well as a \_\_\_\_\_.
- Potential divider
  - Current divider
  - Wheat stone bridge
  - Power divider
- viii. The condition for the wheat stone bridge to be balanced is given by:
- $\frac{R_1}{R_2} = \frac{R_3}{R_4}$
  - $\frac{R_2}{R_1} = \frac{R_3}{R_4}$
- c)  $\frac{R_1}{R_2} = \frac{R_4}{R_3}$
- d) None of above
- ix. The product of resistance and conductance is:
- 1
  - Resistivity
  - Conductance
  - Zero
- x. Unit (S.I) of temperature coefficient of resistivity of a material is:
- K
  - $\text{K}^{-1}$
  - $^\circ\text{C}$
  - $\text{K}^{-2}$

**Q.2 Write the short answers.**

- i. A potential difference is applied across the ends of a copper wire. What is the effect on the drift velocity of free electron by?
- Increasing the potential difference.
  - Decreasing the length and the temperature of the wire.
- ii. Do bends in a wire affect its electrical resistance? Explain.
- iii. Why does the resistance of a conductor rise with temperature?
- iv. What are the difficulties in testing whether the filament of a lighted bulb obeys Ohm's law?
- v. Describe a circuit, which will give a continuously varying potential?
- vi. What is Wheatstone bridge? How can it be used to determine an unknown resistance?
- vii. Write a note on rheostat as a variables resistor.
- viii. State Kirchoff's 2<sup>nd</sup> rule.

**Note: Long questions:**

**Q.3 (a)** define power dissipation in resistors and also derive on expression for it.

**(b)** How many electrons pass through an electric bulb in one minute if the 300 mA current is passing through it?

**Q,4 (a)** Define resistivity name then units. How resistivity depends upon temperature?

**(b)** A rectangular bar of iron is 2.0 cm by 2.0 cm in cross-section and 40 cm long. Calculate its resistance if the resistivity of iron is  $11 \times 10^{-8} \Omega\text{m}$ .