

AAFAQ ACADEMY KASUR

Physics Book II

Chapter (13) NEW
CURRENT ELECTRICITY

Objective + Subjective

Test Session 2014 – Name : _____ Roll No: (in words) _____

OBJECTIVE

Time: 10 Minutes

Marks: 10

Note: Write your roll No. in space provided.

Over-writing, cutting, erasing, using of lead pencils will result into loss of marks.

Encircle the correct answers.

- i. When a pot difference of 4 volt is applied across resistance, 10 J of energy is converted. Find charge flows.
- 0.2. C
 - 2.5 C
 - 5.0 C
 - 10.0 C
- ii. If a charge Q flows through any cross section of the conductor in time t, the current I is:
- $I = Qt$
 - $I = \frac{Q}{t}$
 - $I = \frac{t}{Q}$
 - $I = \frac{Q^2}{t}$
- iii. During electrolysis process, density of CuSO_4 solution.
- Remains constant
 - Decreased
 - Increased
 - None of these
- iv. For non-ohmic devices, the graph between V and I is:
- Not a straight line
 - A straight line
 - A curve
 - All of above
- v. If there is no fourth band, tolerance is shoes as:
- $\pm 10\%$
 - $\pm 20\%$
 - $\pm 5\%$
 - 10%
- vi. The resistivity of _____ decrease with the increase in temp.
- Gold
 - Silver
 - Copper
 - Silicon
- vii. A rheostat can be used as variable resistor as well as a _____.
- Potential divider
 - Current divider
 - Wheat stone bridge
 - Power divider

- viii. The condition for the wheat stone bridge to be balanced is given by:

a) $\frac{R_1}{R_2} = \frac{R_3}{R_4}$

b) $\frac{R_2}{R_1} = \frac{R_3}{R_4}$

c) $\frac{R_1}{R_2} = \frac{R_4}{R_3}$

- d) None of above

- ix. The product of resistance and conductance is:

- a) 1

b) Resistivity

c) Conductance

d) Zero

- x. Unit (S.I) of temperature coefficient of resistivity of a material is:

a) K

b) K^{-1}

c) $^{\circ}\text{C}$

d) K^{-2}

SUBJECTIVE

Time: 30 min.

Marks: 20

Q.2 Write the answer of SIX questions.

- i. A potential difference is applied across the ends of a copper wire. What is the effect on the drift velocity of free electron by?
- Increasing the potential difference.
 - Decreasing the length and the temperature of the wire.
- ii. Do bends in a wire affect its electrical resistance? Explain.
- iii. Why does the resistance of a conductor rise with temperature?
- iv. What are the difficulties in testing whether the filament of a lighted bulb obeys Ohm's law?
- v. Describe a circuit, which will give a continuously varying potential?
- vi. What is Wheatstone bridge? How can it be used to determine an unknown resistance?
- vii. Write a note on rheostat as a variables resistor.
- viii. State Kirchoff's 2nd rule.

Long questions:

- Q.3** (a) What is potentiometer? Give its construction and describe its uses in detail. (5)
- (b) A rectangular bar of iron is 2.0 cm by 2.0 cm in cross-section and 40 cm long. Calculate its resistance if the resistivity of iron is $11 \times 10^{-8} \Omega \cdot \text{m}$. (3)