

# AAFAQ ACADEMY – KASUR

Physics Book II

Chapter (16) NEW

Objective + Subjective

## ALTERNATING CURRENT

Test Session 2014 – Name : \_\_\_\_\_ Roll No: (in words) \_\_\_\_\_

### OBJECTIVE

Time: 10 Minutes

Marks: 10

Note: Write your roll No. in space provided. Over-writing, cutting, erasing, using of lead pencils will result into loss of marks.

Q.1: Encircle the correct answers.

i. If  $V_{rms}$  be the root mean square value of emf then its peak to peak value is given by:

- a)  $\frac{V_{rms}}{\sqrt{2}}$
- b)  $2\sqrt{2}V_{rms}$
- c)  $\frac{2}{\sqrt{2}V_{rms}}$
- d)  $\frac{V_{rms}}{2}$

ii. The value of capacitive reactance is given by:

- a)  $X_c = VI$
- b)  $X_c = \frac{V}{I}$
- c)  $X_c = \frac{I}{V}$
- d) All of above

iii. In case of capacitor, the unit of reactance is:

- a) farad
- b) ohm
- c) newton
- d) All of these

iv. The unit of impedance is:

- a) farad
- b) tesla
- c) ohm
- d) henry

v. The natural frequency of L.C circuit is equal to:

- a)  $\frac{1}{2\pi} \sqrt{\frac{C}{L}}$
- b)  $\frac{1}{2\pi} \sqrt{\frac{L}{C}}$
- c)  $\frac{1}{2\pi\sqrt{LC}}$
- d)  $\frac{\sqrt{LC}}{2\pi}$

vi. The reactance of inductor depends upon:

- a) L
- b)  $\omega L$
- c)  $\omega$
- d) All of the above

vii. The effective value of any sinusoidal alternating current or voltage is:

- a)  $\sqrt{3}$  times its maximum value
- b)  $\frac{1}{\sqrt{2}}$  time its maximum value
- c)  $\sqrt{2}$  times its maximum value
- d) None of the above

viii. At high frequency, the current through a capacitor is:

- a) Small
- b) Infinity
- c) Zero
- d) Large

ix. Radio frequency choke is:

- a) Iron cored
- b) Air cored
- c) Air as well as iron cored
- d) None of these

x. In frequency modulation, the amplitude of carrier waves is:

- a) Increases
- b) Remains constant
- c) Decreases
- d) None of these

### SUBJECTIVE

Time: 30 min.

Marks: 20

Q.2: Write the short answers. (2×6)

- i. A sinusoidal current has rms(effective) value of 10 A. What is the maximum or peak value?
- ii. Name the device that will (a) permit flow of direct current but oppose the flow of alternating current (b) permit flow of alternating current but not the direct current.
- iii. How many times per second will an incandescent lamp reach maximum brilliance when connected to a 50 Hz source?
- iv. A circuit contains an iron-cored inductor, a switch and a D.C. source arranged in series. The switch is closed and after an interval reopened. Explain why a spark umps across the switch contacts?
- v. How does doubling the frequency affect the reactance of (a) an inductor (b) a capacitor?
- vi. Explain the conditions under which electromagnetic waves are produced from a source?
- vii. How the reception of a particular radio station is selected on our radio set?
- viii. Define choke and give its uses.

Note: Long questions:

Q.3 (a) What is series resonance circuit? Describe its properties. Also find the resonance frequency for the circuit. (5)

(b) An alternating current is represented by the equation  $I = 20 \sin 100\pi t$ . Compute its frequency and the maximum and rms values of current. (3)